




















<b>RX-D1</b>		<b>Revision 6.1 de 30-01-2011 EC5ACP Josep</b>				
<b>Orden</b>	<b>Unidades</b>	<b>Referencia en serigrafía del circuito</b>	<b>Valor</b>	<b>marcas posibles en componente</b>	<b>Imagen</b>	
1	22	C9,C2,C5,C7,C20,C22,C24,C25,C27,C28,C33,C35,C36,C38,C42,C43,C45,C46,C48 (+3 en pasabanda)	100nF			
2	22	R13,R15,R17,R21,R26,R28,R29,R32,R35,R38,R41,R42,R43,R44,R47,R48,R49,R50,R52,R56,R60,R74	10k	1002 /103		
3	17	C1,C6,C8,C10,C11,C12,C17,C18,C19,C21,C23,C29,C31,C34,C40,C47,C49	10nF			
4	9	R1,R3,R6,R10,R11,R23,R24,R25,R30	100K	1003 / 104		
5	6	R14,R16,R36,R39,R51	no se ponen			
6	6	R7,R19,R20,R31,R46,R67	3K9	3901/392		
7	5	CE5,CE6,CE9,C14,C15	4u7 16V	LíneaMarca=+		
8	5	U1,U3,U4,U7,U6	LM324D(ADT)	LM324DG		
9	4	R33,R34,R53,R79	330	3300		
10	4	Toroides T37-6 , Pasabanda ( Hay 2 de sobra)	Pasabanda	Amarillo		
11	3	CE1,CE3,CE8	220uF 16V	Largo=+		
12	3	CE2,CE4,CE7	22uF 16V			
13	3	JP1,JP3,JP5 (JP2 y JP4 no se ponen) Hembras	2 de 4 y 1 de 6			
14	3	P1 ( en circuito) ,P2 ( en VOLUMEN) ,P3 ( Cableado para sintonia pasabanda antena)	5k	502	Potenciómetro	
15	3	R45,R2,R9	10	10R0		
16	3	R37,R75,R69	11k	1102		
17	3	cuarzo 4,9152 kHz HC49/U		4.9152		
18	2	C3,C4	220p			
19	2	C13,C32	2n2			
20	2	C30,C26	3n3			
21	2	R5,R12	100	1000		

22	2	R40, R71		24K	2402	
23	2	R8,R65		2K2	2201	
24	2	R78,R73		7K5	7501	
25	2	Switchs ( desplazamiento SLIDE)				
26	2	Hilo cobre estañado soldable, 42cm. Bobina larga de toroides				
27	1	C pasabanda		4p7		
28	1	C16		47pF		
29	1	C37		27nF		
30	1	C39		220nF		
31	1	C41		1n2		
32	1	C44		12nF		
33	1	D1		BAT42WS	B1 ó S1 (2 pines)	
34	1	I1		78L05	78L05	
35	1	conector pines en tira, MACHOS para Pasabanda antena, OFB, y el filtro FI		SL1.025.36Z		
36	1	R4		1M	105 / 1004	
37	1	R22		1k	1001 / 102	
38	1	R18		180K	1803 /184	
39	1	R27		51k1	5112	
40	1	R54		499	4990	
41	1	R55		1k5	1501	
42	1	R57		5K1	5111	
43	1	R58		150	1500	
44	1	R59		9k1	9101	
45	1	R61		36k	3602	
46	1	R62		12k	1202	
47	1	R63		1K3	132	
48	1	R64		30k	3002	
49	1	R66		180	1800	
50	1	R68		240	2400	
51	1	R70		6K2	6201	
52	1	R72		22k	2202	
53	1	R76		220	2200	
54	1	R77		8K2	8201	

55	1 T1		BC547B	BC547B	
56	1 U5		LM386N-4	LM386N-4	
57	1 U2		AD607ARSZ	AD607ARSZ	
58	1 PCB RX-D1 54mm x 120mm. 30 micras,		Circuito principal RX-D1		
59	1 PCB pasabanda		casero		
60	1 C ajustable filtro FI				
61	1 Varicap SVC389 ( Pasabanda)			VJ 784 (3pines)	
62	1 Diodo 1N4007		Entrada alimentación	1N4007	
63	1 Madeja 1,25m de estaño				
64	1 Resistencia PTH ( normal) entre 1K y 10K				
65	1 Hilo cobre cubierta plástico (telefónico). Primario toroides.				
	178				